28th June 2013 AM/FM/Loop Crystal Radio



[http://3.bp.blogspot.com/-W5MoCILOqOU/Uc2WU1CTbbl/AAAAAAAAABNA/hH64_FNxMpo/s436/Screen+Shot +2013-06-23+at+12.06.23+PM.png]

Build a multifunction battery free crystal radio to listen to either AM or FM radio.

You can also use the same radio to connect to a bigger loop coil to get stronger signal for the AM radio instead of relying on the smaller AM coil inside the radio.

Parts you will need:

A Diode that works in high frequency (200Mhz or above, e.g. AA112, 1N34A, 1N48, Iss86 or Iss106.

A Diode that work in AM frequency e.g 1N34A, 1N60, BAT85.

A quadruple PVC Variable capacitor with one end for 2x 20pf, the other end for 2x 140pf.

50pf and 180pf fixed ceramic capacitor

100K 1/4W resistor

33uH Choke coil.


AM radio coil - ferrite rod

3.5mm mono headphone jack

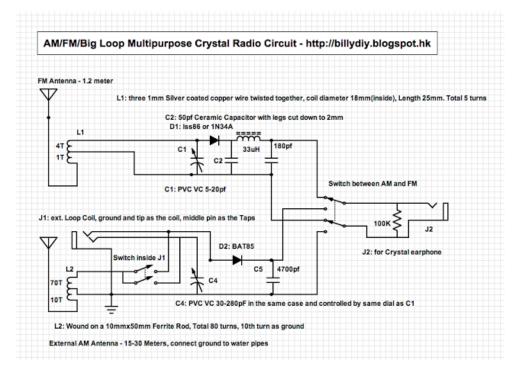3.5mm stereo headphone jack with internal switches (for selecting whether to use the external big loop or the internal coil for AM.


A 2 by 3 switch to select AM or FM.

A high impedance 4K Ohm earphone or a crystal earphone.




[http://2.bp.blogspot.com/--ZAhsy2SRko/Uc2WUu2Gz6I/AAAAAAABM8/czIHQF1iPzI/s855/Screen+Shot+201 3-06-23+at+11.22.21+AM.png]

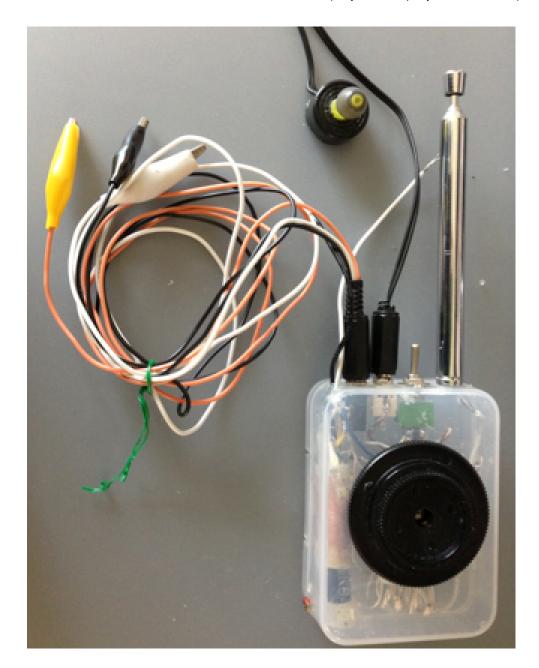To connect to external Loop coil for AM reception instead of using the internal AM coil, connect 3-color crocodile camp to the 3.5mm Stereo jack - white for the tuning, black for ground, yellow for the decoder diode.



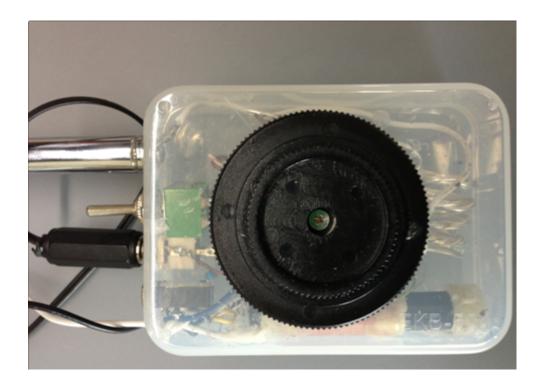[http://3.bp.blogspot.com/-df0Gv1TiXME/Uc2WTw3VL8I/AAAAAAAABMs/hJaPbNYh4uQ/s415/Screen+Shot+2013-06-23+at+1.19.26+PM.png]



[http://2.bp.blogspot.com/-966mXwGZozE/Uc2WVmB2ILI/AAAAAAAABNY/P2KdoM FVIR0/s489/Screen+Shot+2013-06-23+at+12.07.13+PM.png]



 $[http://1.bp.blogspot.com/-\\ UURJiV8VfBY/Uc2WTLqcLFI/AAAAAAAAAABMc/q9_Y7C47Zb8/s1600/IMG_2521.JP\\ G]$



Precompliance Antenna HighEnd Log-Periodic Wideband EMC Antennas from 1Hz to 40GHz Go to aaronia.com/antennas

Add a comment

